

Shunt Calibration Calculation Example

$$\text{If } \frac{1}{R_{gsh}} = \frac{1}{R_g} + \frac{1}{R_{sh}} \quad \text{Then } R_{sh} = \frac{R_g \times R_{gsh}}{R_g - R_{gsh}}$$

where:

$R_g = 350$ = Resistance of the strain gage, ohms

2000 ppm = 0.002 = Full scale deviation of the meter

$D = 350 \times 0.002 = 0.7$ = Corresponding resistance change, ohms

$R_{gsh} = 350 - 0.7 = 349.3$ = Corresponding resistance of the shunted gage

R_{sh} = Resistance of a shunt R_{sh} causing the change D

$$R_{sh} = \frac{(350 \times 349.3)}{(350 - 349.3)} = 174,650 \text{ ohms}$$